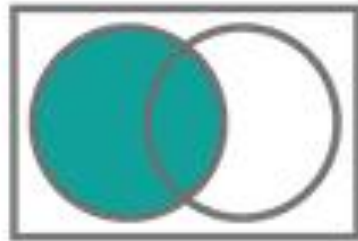


2.5 Boolean Functions


Venn Diagrams of Some Basic Functions



A



B

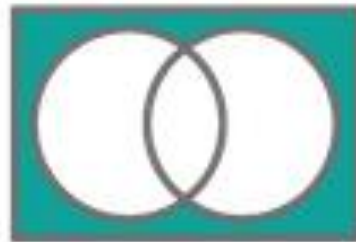

A NOR B



A NAND B








A XOR B



A XNOR B

4-Input AND Functions

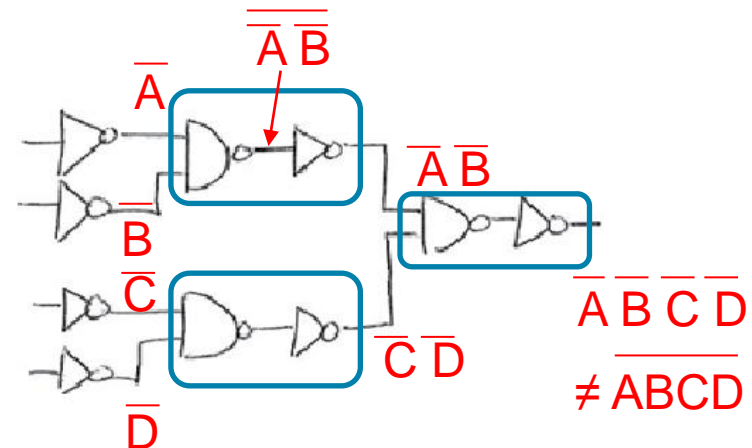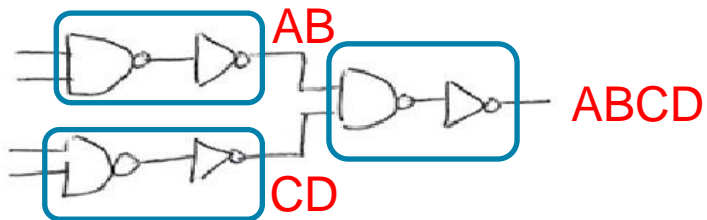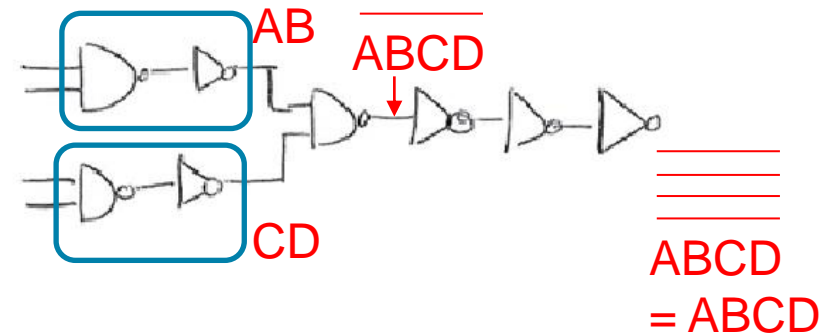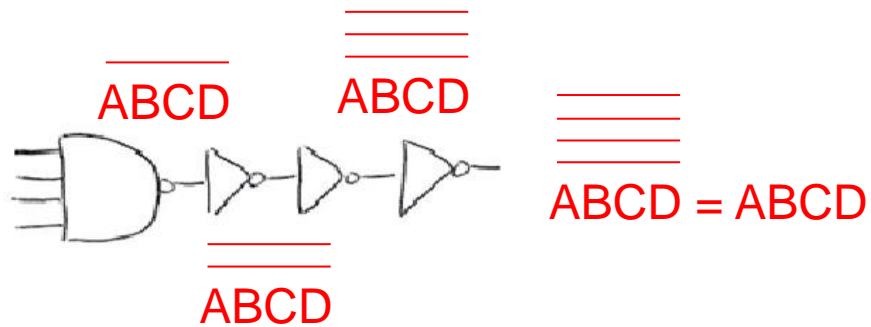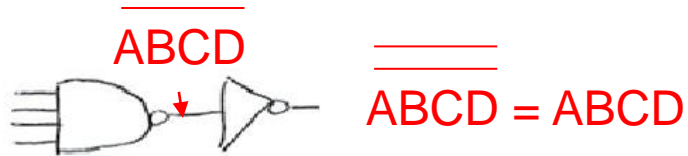

2.4 (c) Reduce to one literal

$$A'B(D' + C'D) + B(A + A'CD)$$

Factor

$$A'BD' + A'BC'D + BA + BA'CD$$

factor out B

$$B(A'D' + A'C'D + A + A'CD)$$

factor out A'D

$$B(A'D' + A'D(C' + C) + A)$$

$$B(A'D' + A'D + A)$$

factor out A

$$B(A'(D' + D) + A)$$

$$B(A' + A)$$
$$B$$

2.6 Canonical and Standard forms

Minterms/maxterms

- A shorthand notation for describing functions
- Any Boolean function can be represented by a truth table with 2^N rows (N variables)
- The literal combinations for 1's are called minterms and are grouped together with OR functions
- The complemented literal combinations for 0's are called maxterms and are grouped together with AND functions

2.6 Minterms/maxterms

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

The **minterms** of the XOR gate are:

$$A'B + AB'$$

Can be written as $m_1 + m_2$

$X = m_1 + m_2$ (minterm 1 OR minterm 2)
(product of sums)

The **maxterms** of the XOR gate are:

(Note how maxterms are written: don't sum the zeros)

$$(A + B)(A' + B')$$

Can be written as M_0M_3

$X = M_0M_3$ (maxterm 0 AND maxterm 3)
(sum of products)

2.6 Minterms/maxterms

Table 2.3
Minterms and Maxterms for Three Binary Variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

2.6 Minterms/maxterms

Table 2.4
Functions of Three Variables

x	y	z	Function f_1	Function f_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$f_1 = m_1 + m_4 + m_7$$

$$= x'y'z + xy'z' + xyz$$

$$f_2 = m_3 + m_5 + m_6 + m_7$$

$$= x'yz + xy'z + xyz' + xyz$$

$$f_1 = M_0 M_2 M_3 M_5 M_6$$

$$= (x+y+z)(x+y'+z)(x+y'+z')(x'+y'+z)(x'+y'+z)$$

$$f_2 = M_0 M_1 M_2 M_4$$

$$= (x+y+z)(x+y+z')(x+y'+z)(x'+y+z)$$

2.6 Canonical and Standard forms minterms/maxterms


Example of a digital logic function
seat-belt interlock system

	W	X	F	
all	0	0	0	W - foot on brake
combinations	0	1	0	X - driver seat belt on
of two	1	0	0	
variables	1	1	1	

$$F = M_3 = WX$$

Both a

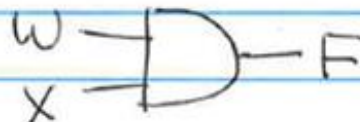foot must be on the brake and
the driver seat belt must be on



2.6 Canonical and Standard forms

Minterms/maxterms

Example of a digital logic function
seat-belt interlock system


WXYZ	F	Y - door shut	W - foot on brake	X - driver seat belt on
0000	0			
0001	0			
0010	0			
0011	0			
0100	0			
0101	0			
0110	0			
0111	0			
1000	0			
1001	0			
1010	0			
1011	0			
1100	0			
1101	0			
1110	0			
1111	1			

N=4 variables
 2^N rows of the truth table

→ All four conditions must be true for the car to start

truth table = representation of function

minterms = $F = m_{15} = WXYZ$

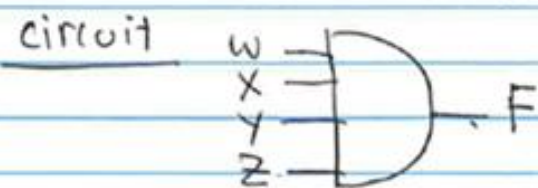

2.8 Digital Logic Gates







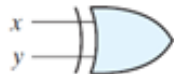
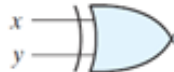
Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = x \cdot y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	
NAND		$F = (xy)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= (x \oplus y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

FIGURE 2.5
Digital logic gates

Truth Table

truth table - defines a function

2^n rows for N variables

	A	B	C	\neg
m_0	0	0	0	0
m_1	0	0	1	1
m_2	0	1	0	1
m_3	0	1	1	0
m_4	1	0	0	0
m_5	1	0	1	0
m_6	1	1	0	0
m_7	1	1	1	0

minterms

$$y = \sum (m_1, m_2)$$

$$= m_1 + m_2 \quad (\text{or})$$

$$= \bar{A} \bar{B} C + \bar{A} B \bar{C}$$

maxterms

$$y = \prod (M_0 M_3 M_4 M_5 M_6 M_7) \quad (\text{AND})$$

$$= M_0 M_3 M_4 M_5 M_6 M_7$$

$$= (A+B+C) (A+\bar{B}+\bar{C}) (\bar{A}+B+C)$$

m_0


m_3

m_4

.....

(change operation
& complement
variable)

Convert Representations of a Function

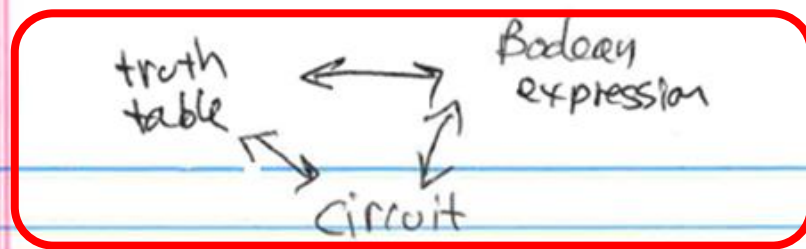


$$Y = (A+B)C + B$$

3 variables $\Rightarrow 2^3 = 8$ rows what is the B

A	B	C	(A+B)	(A+B)C	$Y = (A+B)C + B$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	1	1

↑
AND
these
columns
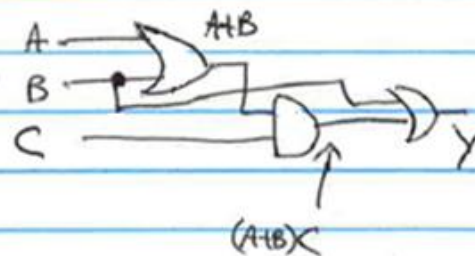
$$\begin{aligned}
 Y &= m_2 + m_3 + m_5 + m_6 + m_7 \\
 &= \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C \\
 &\quad + ABC + ABC
 \end{aligned}$$



what is the truth table?
what does the circuit look like?
what is the Boolean expression?

$$Y = (\overline{A+B})C$$

what is the truth table?


what does the circuit look like?

A B C	$\overline{A+B}$	$Y = (\overline{A+B})C$
0 0 0	1	0
0 0 1	1	1
0 1 0	0	0
0 1 1	0	0
1 0 0	0	0
1 0 1	0	0
1 1 0	0	0
1 1 1	0	0

A B	$\overline{A+B}$
0 0	1
0 1	0
1 0	0
1 1	0

NOR

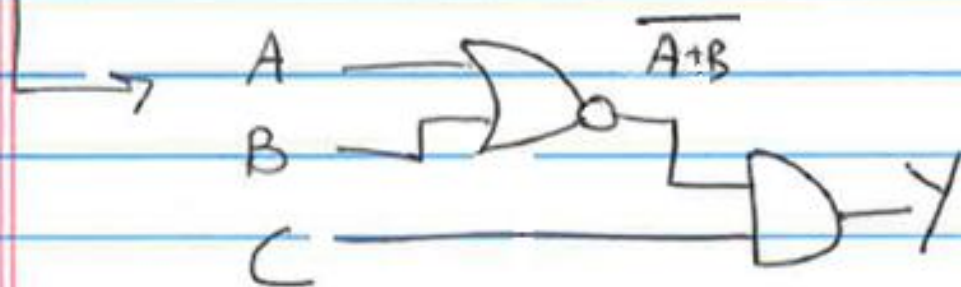Y can be written as $Y = M_1$
 $= \overline{A} \overline{B} C$



2.17a Obtain the truth table

$$y = (b + cd)(c + bd)$$

bcd	cd	(b+cd)	bd	(c+bd)	y
000	0	0	0	0	0
001	0	0	0	0	0
010	0	0	0	1	0
011	1	1	0	1	1
100	0	1	0	0	0
101	0	1	1	1	1
110	0	1	0	1	1
111	1	1	1	1	1

↑
AND
↑


Q.17(b) $Y = (cd + b'c + bd')(b+d)$

bcd	cd	$b'c$	bd'	$(cd + b'c + bd')$	$(b+d)$	Y
000	0	0	0	0	0	0
001	0	0	0	0	1	0
010	0	1	0	1	0	0
011	1	1	0	1	1	1
100	0	0	1	1	1	1
101	0	0	0	0	1	0
110	0	0	1	1	1	1
111	1	0	0	1	1	1

↑ AND ↑

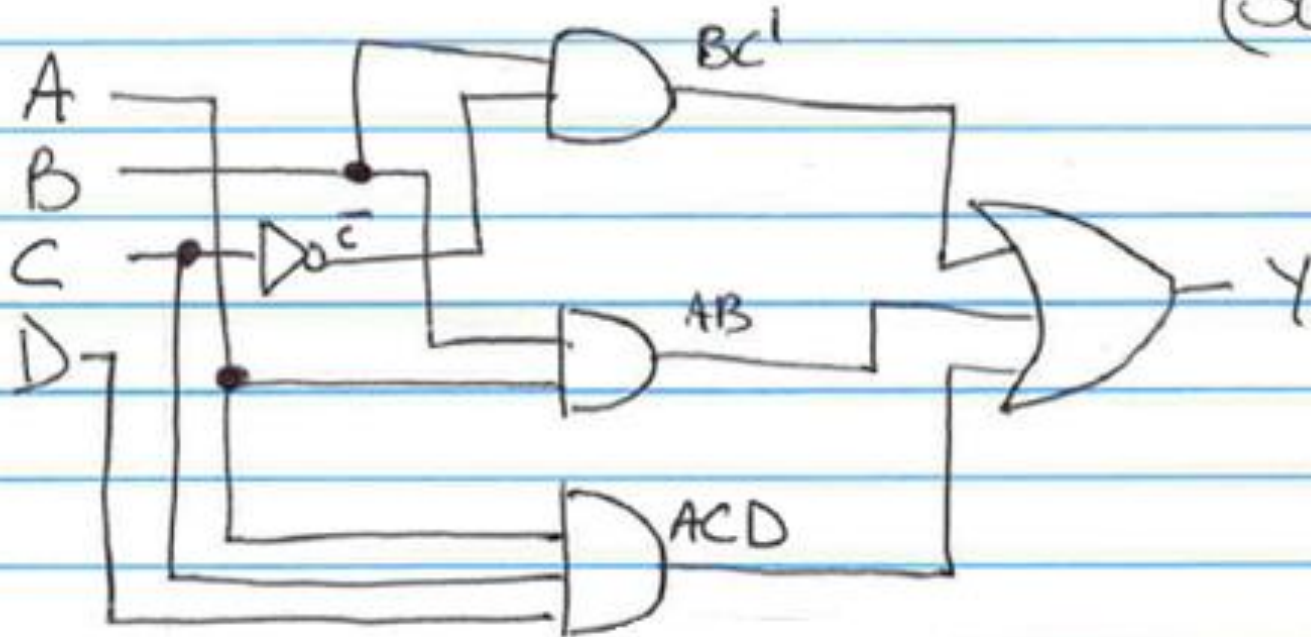
2.23 Draw the logic diagram for the following expression without simplifying

$$(a) Y = BC' + AB + ACD \Rightarrow \text{sum-of-products form (SOP)}$$




2.23

$$(d) Y = A + CD + (A + D')(C' + D)$$

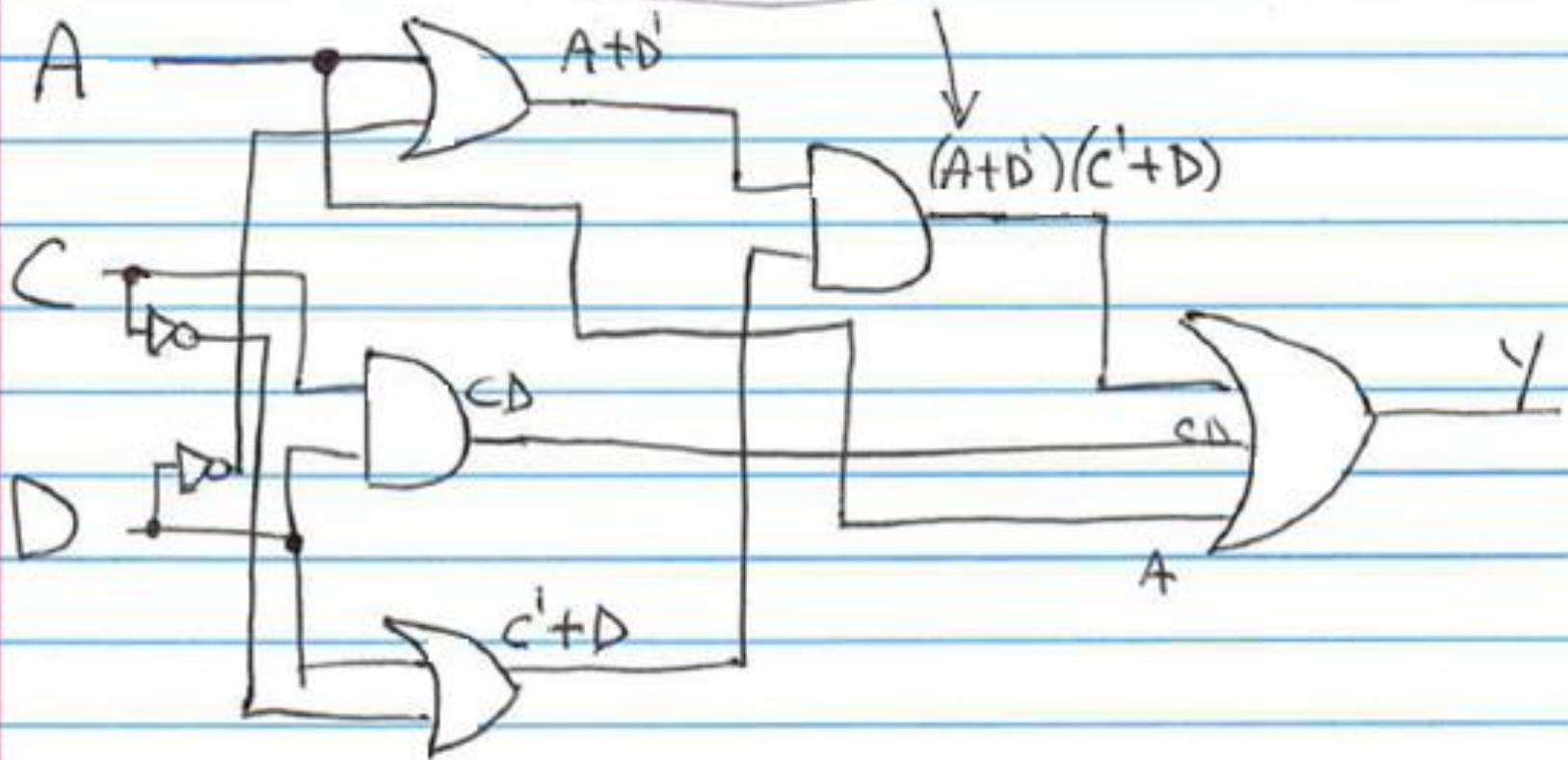

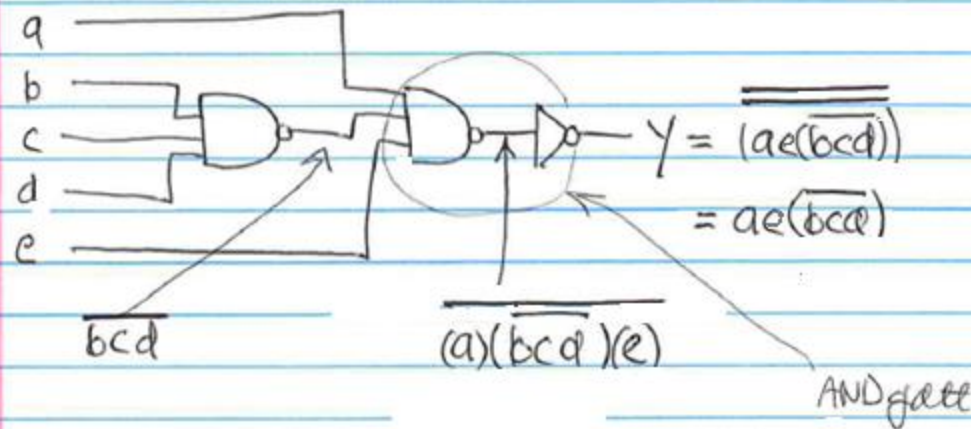2.28 Write the Boolean expression and truth table
(a) describing the outputs of the circuit




truth table

a	b	c	d	e	(bcd)	ae	$ae(\overline{b}bcd)$
0	0	0	0	0	1	0	0
0	0	0	0	1	1	0	0
0	0	0	1	0	1	0	0
0	0	0	1	1	1	0	0
0	0	1	0	0	1	0	0
0	0	1	0	1	1	0	0
0	0	1	1	0	1	0	0
0	0	1	1	1	1	0	0
0	1	0	0	0	1	0	0
0	1	0	0	1	1	0	0
0	1	0	1	0	1	0	0
0	1	0	1	1	1	0	0

2.28(b)

$$a \oplus (c + d + e)$$

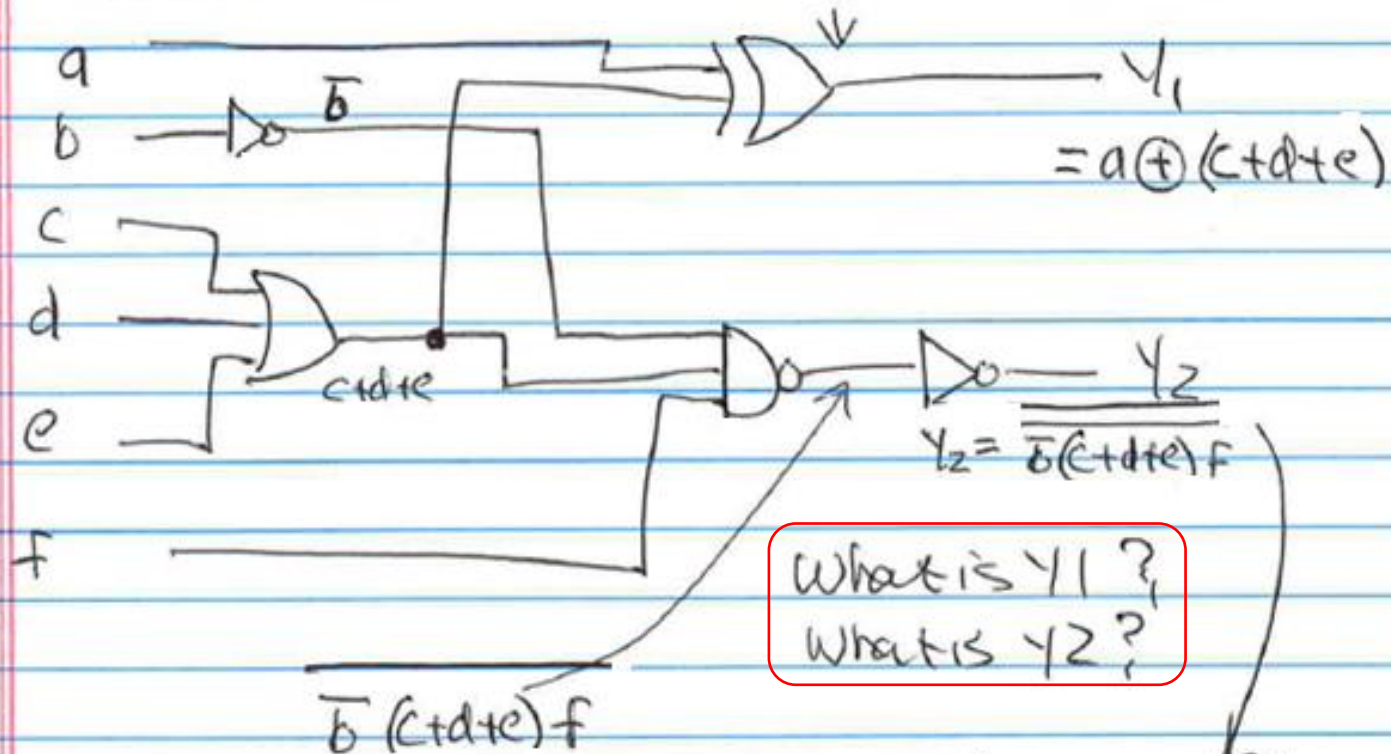

What is Y_1 ?
What is Y_2 ?

$$= a \oplus (c + d + e)$$

$$Y_2 = \overline{b}(c + d + e)f$$

What is Y_1 ?
What is Y_2 ?

complements cancel.

$$Y_2 = \overline{b}(c + d + e)f$$

2.20 Find the complement of the following functions in sum-of-minterms form

(a) $F(A, B, C, D) = \sum (2, 4, 7, 10, 12, 14)$

A	B	C	D	F	\bar{F}	$\bar{F}(A, B, C, D) = \sum (0, 1, 3, 5, 6, 8, 9, 11, 13, 15)$
0	0	0	0	0	1	
0	0	0	1	0	1	
0	0	1	0	1	0	
0	0	1	1	0	1	
0	1	0	0	1	0	
0	1	0	1	0	1	
0	1	1	0	0	1	
0	1	1	1	0	1	
1	0	0	0	0	1	
1	0	0	1	0	1	
1	0	1	0	1	0	
1	0	1	1	0	1	
1	1	0	0	1	0	
1	1	0	1	0	1	
1	1	1	0	1	0	
1	1	1	1	0	1	

(b) $F(x, y, z) = \prod (3, 5, 7)$

x	y	z	F	\bar{F}	$\bar{F} = \sum (3, 5, 7)$
0	0	0	1	0	
0	0	1	1	0	
0	1	0	1	0	
0	1	1	0	1	
1	0	0	1	0	
1	0	1	0	1	
1	1	0	1	0	
1	1	1	0	1	

2.29

True or False

Use Boolean algebra

$$X'Y' + X'Z + X'Z' \stackrel{?}{=} X'Z' + Y'Z' + X'Z$$

$$X'(Y' + Z + Z') = X'Z' + Y'Z' + X'Z$$

$$X' : X'(Z' + Z) + Y'Z'$$



$$X' = X' + Y'Z' \quad \text{Not equal}$$

Or a truth table


X	Y	Z	X'	Y'Z'	X' + Y'Z'
0	0	0	1	1	1
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	0

↑ ↑
Not equal

Boolean Expressions from Circuits

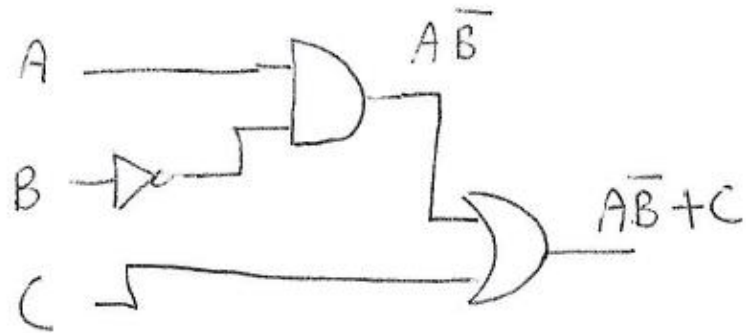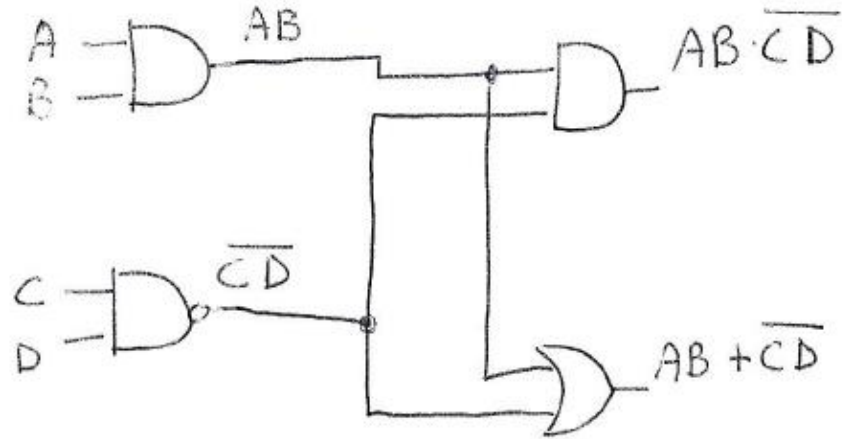


Boolean Expressions from Circuits

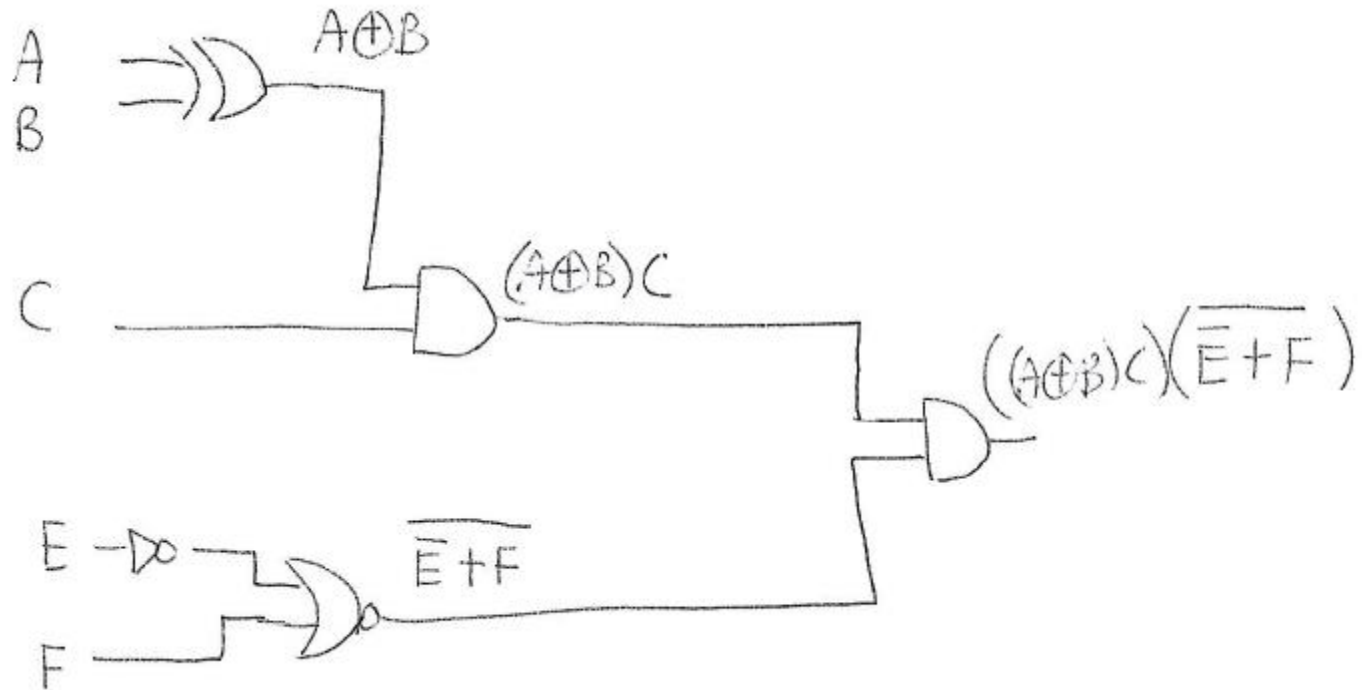


2 13 Draw the logic diagram to implement the following Boolean expressions.

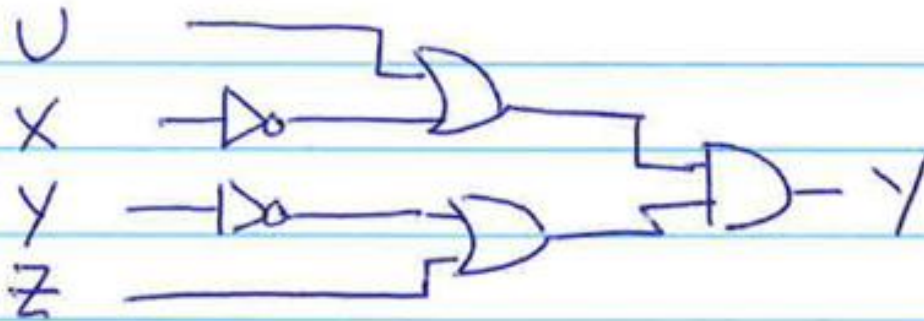
(a) $y = (u + x') (y' + z)$ Bad notation – y should not be used as and input and output




$$y = (u \oplus y)' + x$$

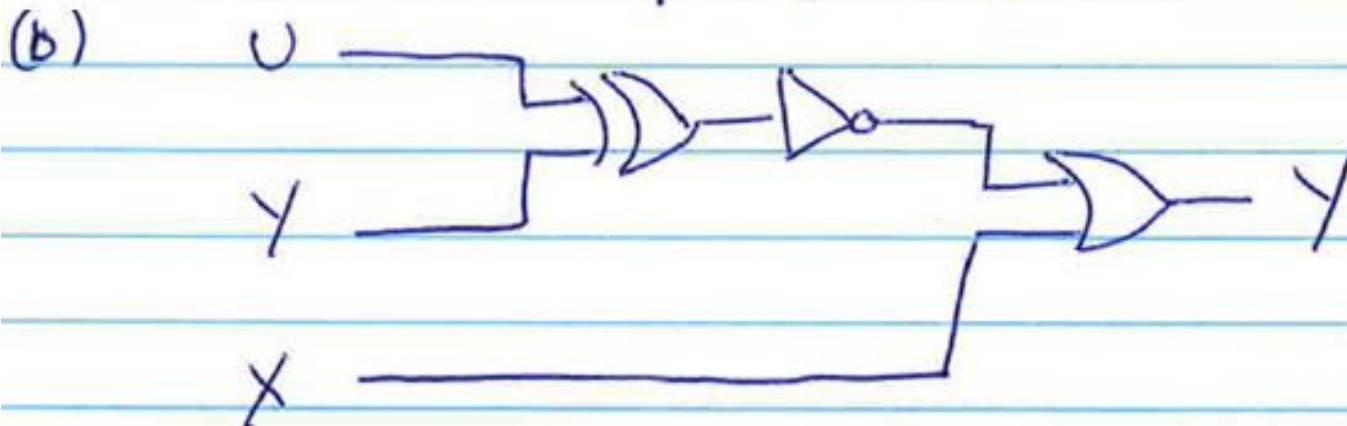

2.13(c) $y = (v' + x')(y + z')$

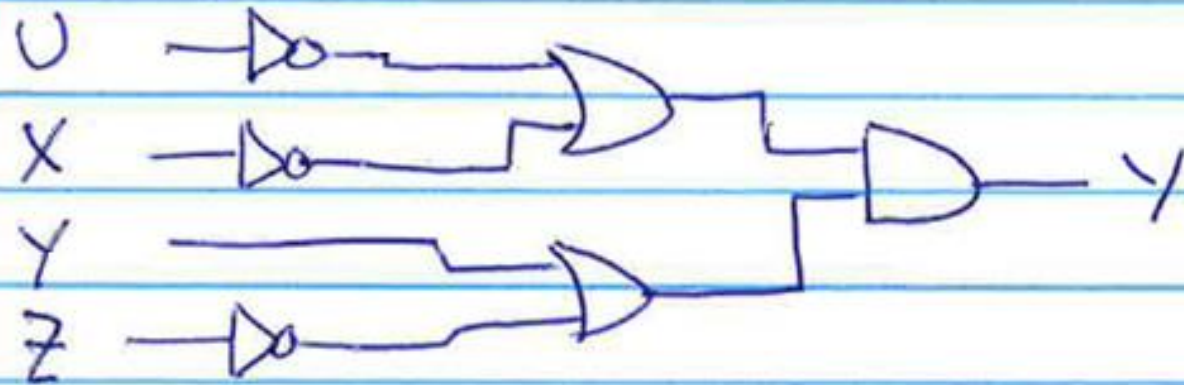


2.13(d) $y = v(x \oplus z) + y'$

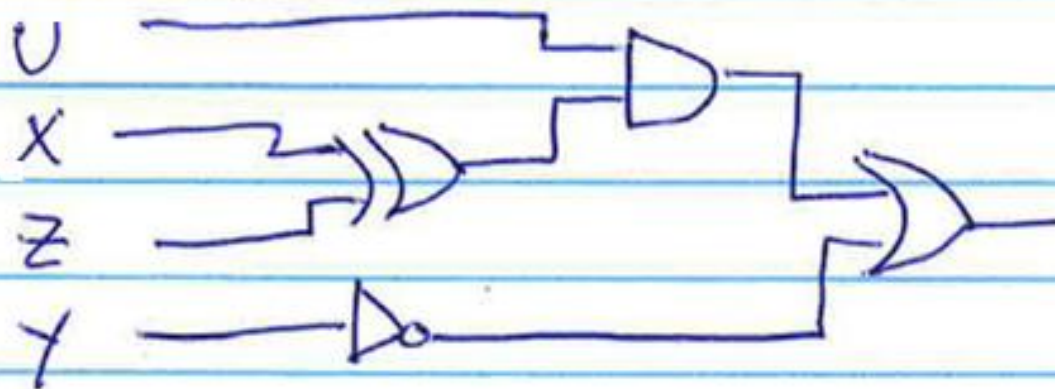

2.13(c) $Y = U + YZ + UXY$

U Y Z X

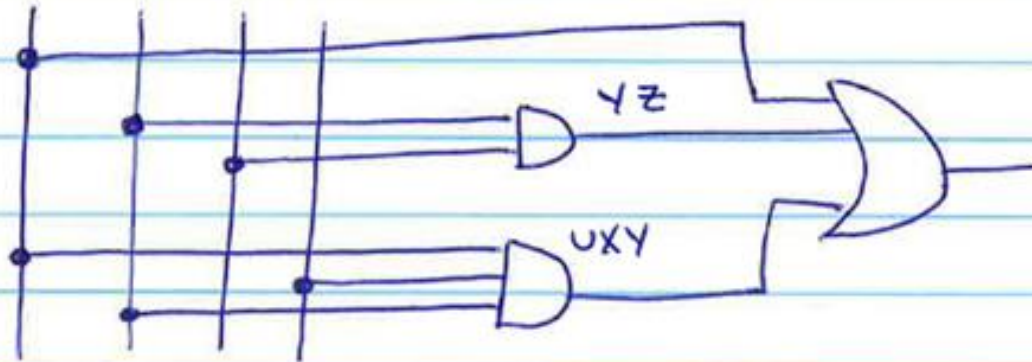

2.13(f) $Y = U + X + X'(U + Y')$

