2.17 (b) Find the truth table y= (cd + b'c + bd') (6+0) cd cd btd

1 AND I

2.30 Write the following in sum-of-products-form F = (6+a)(a'+b'+c') = ba' + bb' + bc + da' + db' + dc

what are the minterms of F?

| The state of the s | |
|--|---|
| a b cd ba' bc da' db' dc F | |
| 0000 0 0 0 0 0 0 | F= E(1,3,4,5,6,7,9,11,14,15) |
| 00 10 00 00 00 00 00 00 00 00 00 00 00 0 | = m, +m3 +m4 +m5 +m6 +m7 |
| 0 1 0 1 1 1 0 1 0 0 0 | + m9 + m1 + m1+ +m,5 |
| | |
| 100100000000000000000000000000000000000 | = a'bid + a'bid + a'bid + a'bid + a'bid |
| 1011000000000000 | + a'ted + a b'ed + a b'ed + a b ed' |
| 1 1 0 0 0 0 0 0 0 0 0 | |
| | + abid |
| | |

7.31 Write in product-of-soms form F = a'b + a'c' + abc

| abc | 1 a'b | a'c' | abc | E | |
|---------|-------|------|-----|----|---------------|
| 000 | 0 | | 0 | | F=TT(1,4,5,6) |
| 001 | 0 | 0 | 0 | 0 | |
| 010 | | (| 0 | 1 | = M, M4M 5 M6 |
| 011 | 1 | 0 | 0 | 1 | |
| 100 | 0 | 0 | 0 | 0 | |
| 101/ | 0 | 0 | 0 | 0 | |
| 110 | 0 | 0 | 0 | 0 | |
| 1 1 1 1 | 0 | 0 | 1 | 11 | |

| \rightarrow | = +> | X+; | Ī | char | ige ope | vator t variabl | es. |
|--------------------------|-----------------|------------|------------------------------|-----------------|----------------|--------------------|-------------|
| X Y 0 0 1 1 1 | X Y 1 1 0 1 0 1 | 7 + 7 | - - | <u></u> | = [*] | 3 | > |
| X | +1: | = X 7 | C | hange omplen | operato | ri ables | |
| 1 0 0 0 1 0 1 1 | X+V | F.X OOO | X_* | 0 | _ × | | |

• Simplify
$$C + \overline{BC}$$

$$C + \overline{BC}$$

$$C + (\overline{B} + \overline{C})$$

$$(C + \overline{C}) + \overline{B}$$

$$I + \overline{B}$$

$$I$$

Simplify
$$\overline{AB}(\overline{A} + B)$$

$$\overline{AB}(\overline{A} + B)$$

$$(\overline{A} + \overline{B})(\overline{A} + B)$$

$$\overline{A} + \overline{A}B + \overline{A}\overline{B}$$


$$\overline{\mathbf{A}}$$


$$F_{a} = ABC + DEF$$

$$= ABC \cdot DEF$$

$$= (ABC) (D+E+F)$$

$$= (AB) (D) (EF)$$

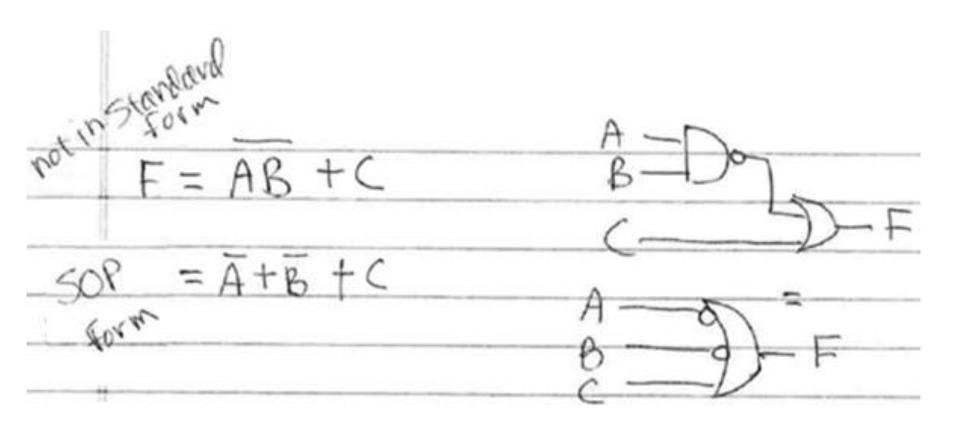

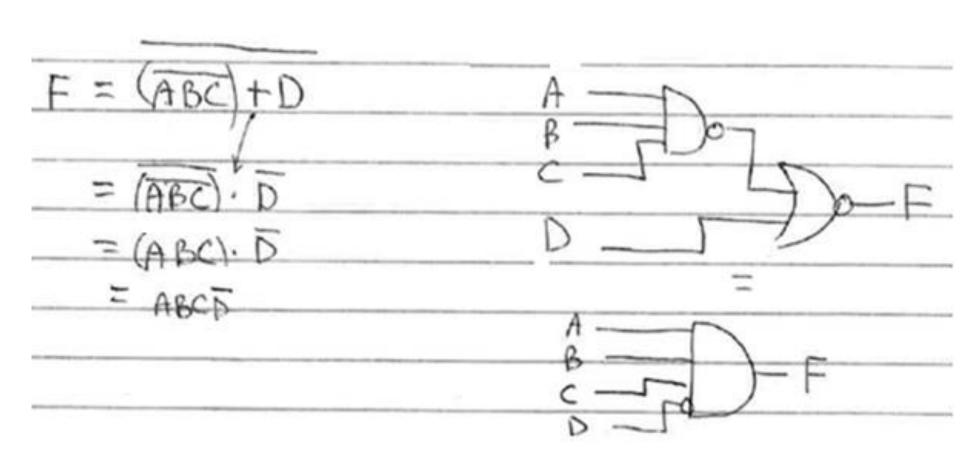


$$F_{_{1}} = \overline{(\overline{X \cdot \overline{Y}}) \cdot (\overline{Y} + Z)}$$

$$\mathsf{F}_{_{1}}=(\overline{\overline{\mathsf{X}\cdot\overline{\mathsf{Y}}}})+(\overline{\overline{\mathsf{Y}}+\mathsf{Z}})$$

$$F_{1} = (X \cdot \overline{Y}) + (\overline{\overline{Y}} \cdot \overline{Z})$$

$$F_{_{1}}=(X\cdot\overline{Y})+(Y\cdot\overline{Z})$$

$$F_1 = X\overline{Y} + Y\overline{Z}$$

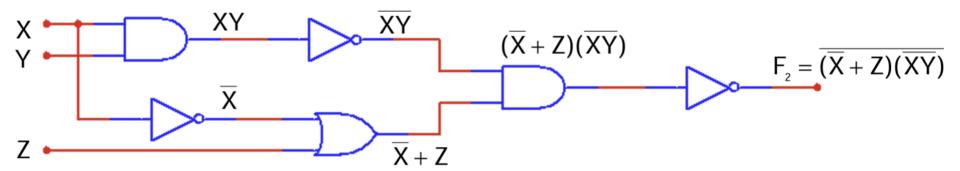

$$F_2 = \overline{(\overline{X} + Z)(\overline{XY})}$$

$$F_2 = (\overline{\overline{X} + Z}) + (\overline{\overline{XY}})$$

$$F_2 = (\overline{\overline{X} + Z}) + (XY)$$

$$F_2 = (\overline{\overline{X}} \overline{\overline{Z}}) + (XY)$$

$$F_2 = (X \overline{Z}) + (XY)$$

$$F_2 = X \overline{Z} + X Y$$

Prob 2.24

$$F = (A \oplus B)$$

$$= (AB + AB)$$

$$= (AB) (AB)$$

$$= (AB) (A+B)$$


$$= (A+B) (A+B)$$


$$= (AB+AB) = (A+B)$$


$$= (AB+AB) = (A+B)$$

$$= (AB+AB) = (A+B)$$

$$= (AB+AB) = (A+B)$$

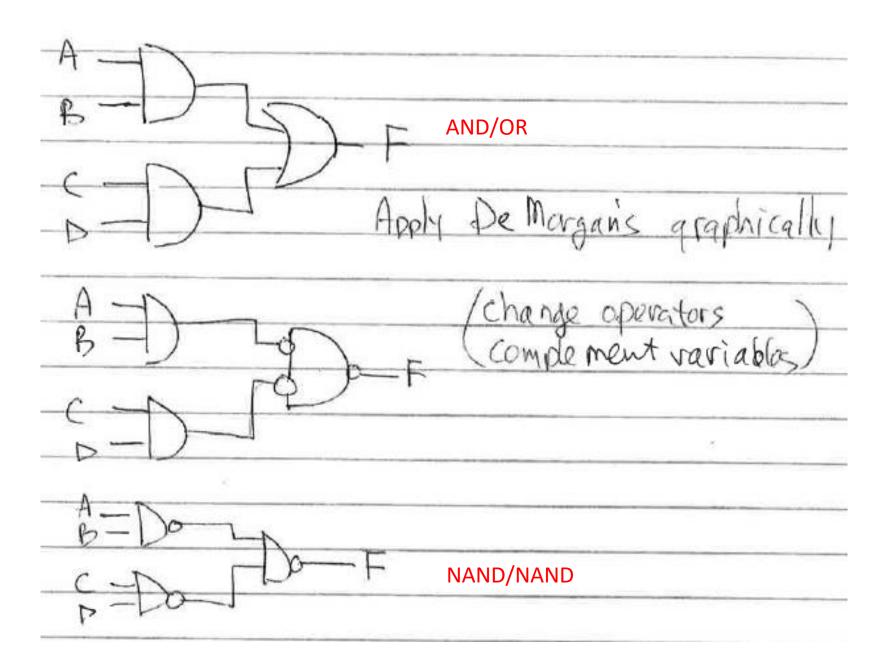

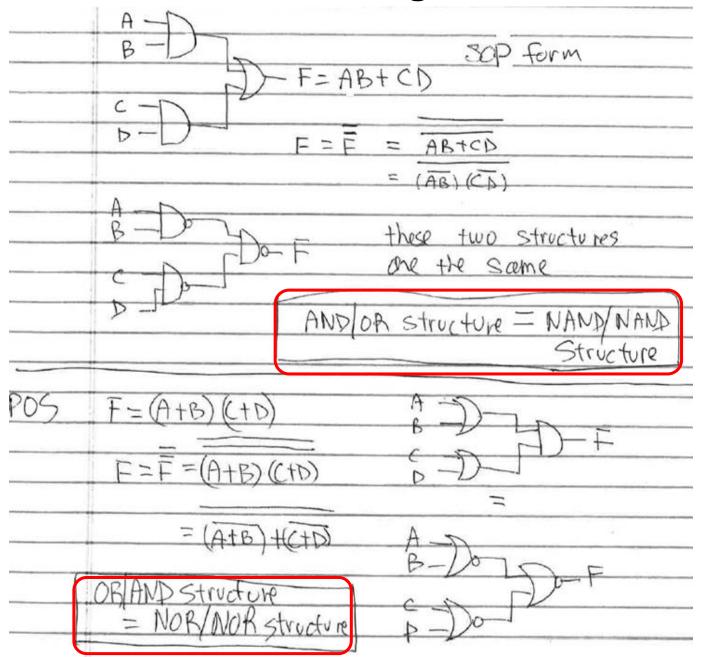

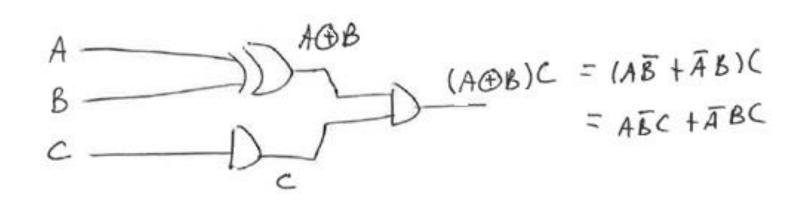

A $A = A + (A + B) \oplus C$ = A + (A + B) C = A + (A + B) C

= B(A OC)

$$Y = (\overline{AB+C} + D)(BC+\overline{D})$$

$$= (\overline{AB+C} + D) + (BC+\overline{D})$$

$$= (\overline{AB+C} + D) + (BC-\overline{D})$$

$$= (\overline{AB+C} + D) + (\overline{B}+\overline{C})D$$

$$= (\overline{A+B})\overline{C} + D) + \overline{B}D + \overline{C}D$$

$$= \overline{AC} + \overline{BC} + D + \overline{B}D + \overline{C}D$$

$$= \overline{AC} + \overline{BC} + D(1 + \overline{B}+\overline{C})$$

$$= \overline{AC} + \overline{BC} + D$$

$$Y = (A + B\overline{c}) \oplus (A + c)$$

ABOB & AC